

IITB-CPU: A 16 bit CPU

Project report for *Indian Institute of Technology, Bombay*
EE224: Digital Systems

Instructor: Prof. Virendra Singh

Abhiruchi Kotamkar	Arya Vishe	Shlesh Gholap	Shobhit Maheshwari
210070043	21d070018	210070080	210070081

November 30, 2022

Contents

1	Introduction	2
2	States	2
2.1	Description	2
2.2	ADD and NAND	2
2.3	ADI	3
2.4	BEQ	3
2.5	JAL and JLR	3
2.6	LHI	4
2.7	LW and SW	4
2.8	LM and SM	4
3	Transition Logic and Control Signals	5
4	Finite State Machine	7
5	Datapath	7
5.1	Components used in Data Path	8
5.2	Code implementation of Data Path	8
6	Testing	8
6.1	CPU definition	8
6.2	Testing Code	8
7	Making a for loop	14
8	Conclusion	14

1 Introduction

The IITB-CPU implements 15 instructions and utilises 8 programmer registers, of which register 7 (*R7*) is used as a program counter or an instruction register. Internally, 15 states are used to implement these instructions and are described in the following section.

2 States

2.1 Description

The states and a short description of each is given below:

State 1	Read from memory and increment PC
State 2	Read R type instruction
State 3	Perform ALU-specific operation
State 4	Update programmer registers
State 5	Read ADI type instruction
State 6	Read LW, SW type instruction
State 7	Read from memory
State 8	Store into memory
State 9	Read LHI type instruction
State 10	Branch to PC+Immediate
State 11	Store PC in Register A
State 12	Branch to Register B
State 13	Load from memory to register
State 14	Update input to priority encoder
State 15	Load from register to memory

2.2 ADD and NAND

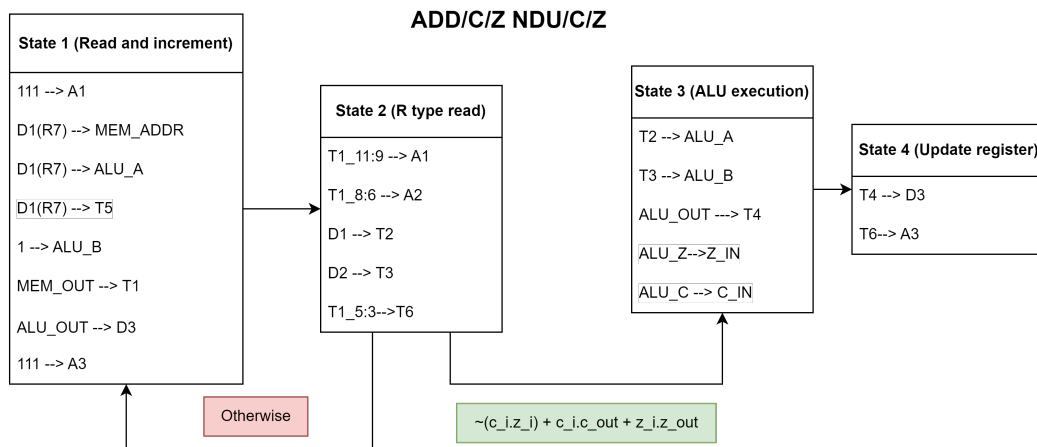


Figure 1: ADD/C/Z and NDU/C/Z instruction state-flow

2.3 ADI

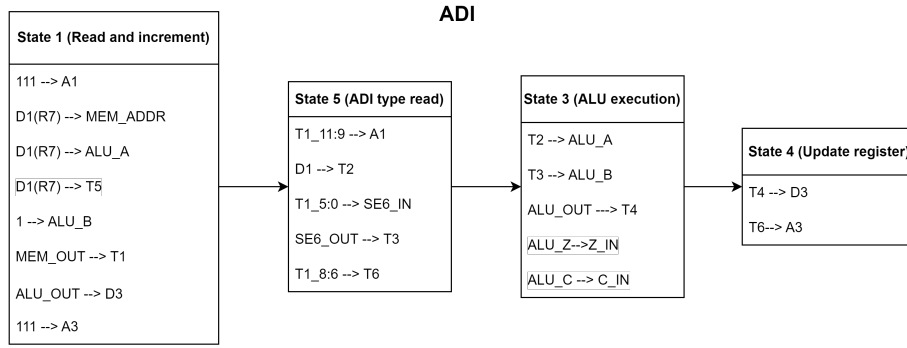


Figure 2: ADI instruction state-flow

2.4 BEQ

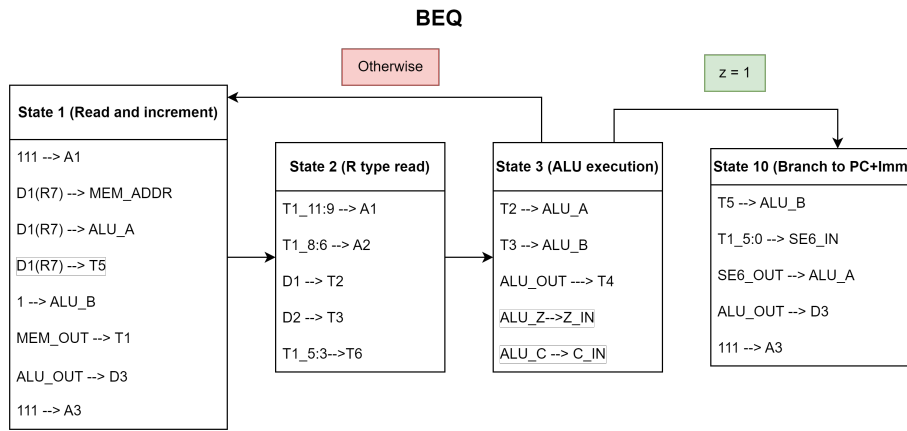


Figure 3: BEQ instruction state-flow

2.5 JAL and JLR

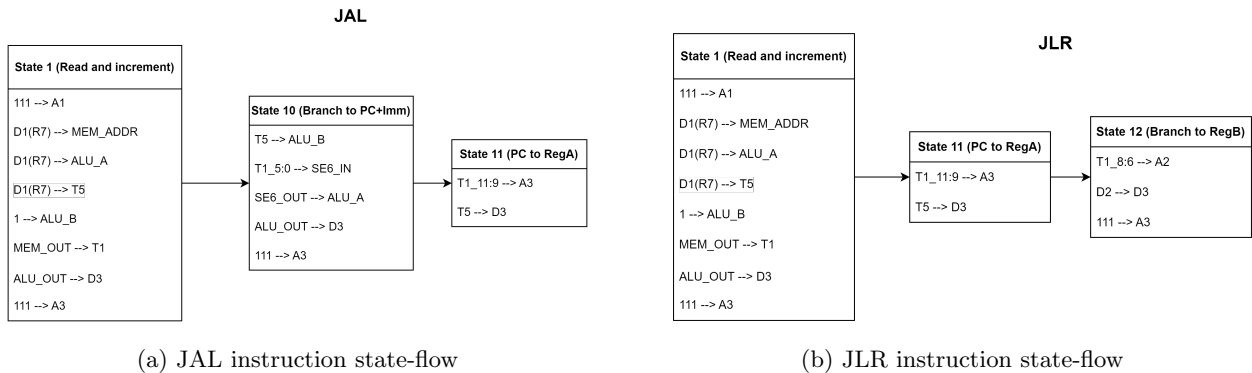


Figure 4: Combined state-flows of JAL and JLR

2.6 LHI

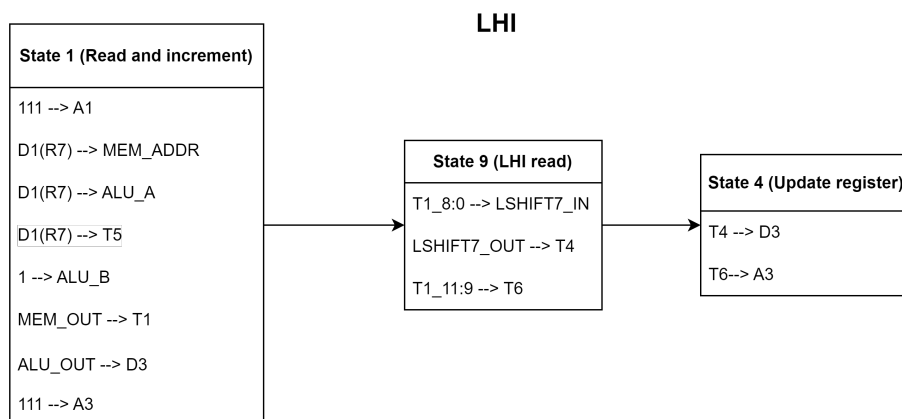


Figure 5: LHI instruction state-flow

2.7 LW and SW

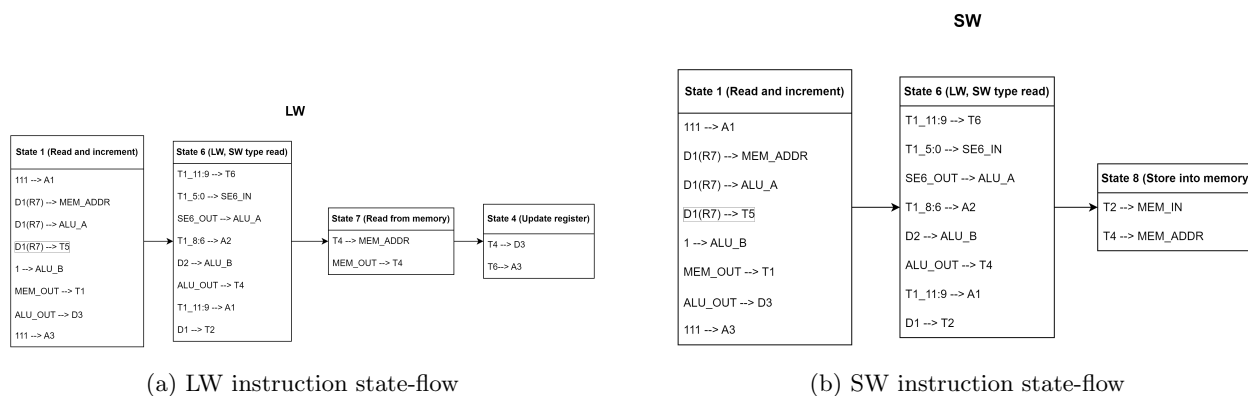


Figure 6: Combined state-flows of LW and SW

2.8 LM and SM

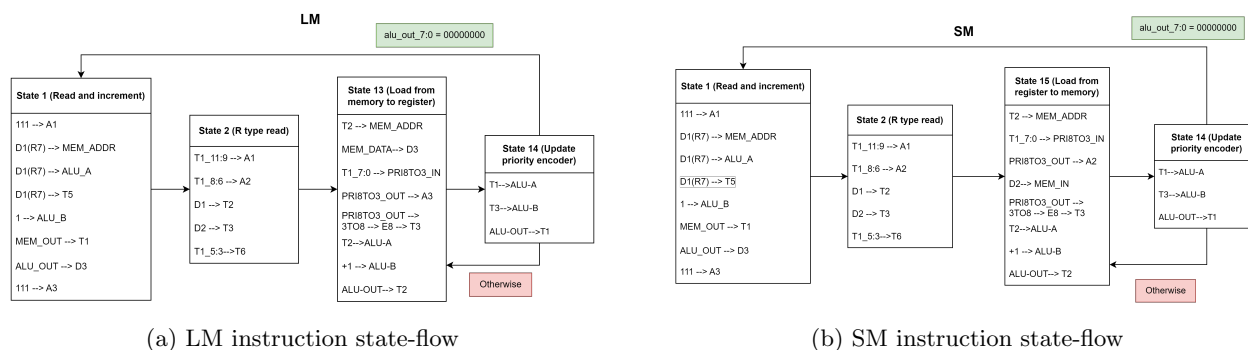


Figure 7: Combined state-flows of LM and SM

3 Transition Logic and Control Signals

Using behavioural modelling, state transition can be facilitated based on the values of:

1. Op. Code (4 most significant bits of instruction)
2. C and Z priority bits (2 least significant bits of instruction)
3. C and Z flag (contents of flag register)

The following control signals had to be defined:

- Memory read enable (M_RD)
- Memory write enable (M_WR)
- Programmer register write enable (PR_WR)
- Temporary register 1 write enable (T1_WR)
- Temporary register 2 write enable (T2_WR)
- Temporary register 3 write enable (T3_WR)
- Temporary register 4 write enable (T4_WR)
- Temporary register 5 write enable (T5_WR)
- Temporary register 6 write enable (T6_WR)
- Z flag write enable (Z_EN)
- C flag write enable (C_EN)
- ALU select signal (ALU_SELECT_0 and ALU_SELECT_1)

The MUX select signals have been defined by accounting for all possible choices in each state.


State	PR_WR	M_WR	M_RD	T1_WR	T2_WR	T3_WR	T4_WR	T5_WR	T6_WR	Z_EN	C_EN	ALU1	ALU0
1	1	0	1	1	0	0	0	1	0	0	0	0	0
2	0	0	0	0	1	1	0	0	1	0	0	0	0
3	0	0	0	0	0	0	1	0	0	$(\text{lop}[3]) * (\text{lop}[2]) * (\text{lop}[1] * \text{op}[0])$	$(\text{lop}[3]) * (\text{lop}[2]) * (\text{lop}[1])$	$\text{lop}[3] * \text{lop}[2] * \text{op}[1] * \text{lop}[0]$	$\text{op}[3] * \text{op}[2]$
4	1	0	0	0	0	0	0	0	0	0	0	0	0
5	0	0	0	0	1	1	0	0	1	0	0	0	0
6	0	0	0	0	1	0	1	0	1	$\text{lop}[3] * \text{op}[2] * \text{lop}[1] * \text{lop}[0]$	0	0	0
7	0	0	1	0	0	0	1	0	0	0	0	0	0
8	0	1	0	0	0	0	0	0	0	0	0	0	0
9	0	0	0	0	0	0	1	0	1	0	0	0	0
10	1	0	0	0	0	0	0	0	0	0	0	0	0
11	1	0	0	0	0	0	0	0	0	0	0	0	0
12	1	0	0	0	0	0	0	0	0	0	0	0	0
13	1	0	1	0	1	1	0	0	0	0	0	0	0
14	0	0	0	1	0	0	0	0	0	0	0	0	1
15	0	1	0	0	1	1	0	0	0	0	0	0	0

Table 2: State-wise control signals

Present State	Next State	Condition
State 1	State 2	$!(op[3]) * !(op[2]) * !(op[0]) + (op[2] * op[1]) + (op[3] * op[2])$
	State 5	$!(op[3]) * !(op[2]) * !(op[1]) * op[0]$
	State 6	$!(op[3]) * op[2] * !(op[1])$
	State 9	$!(op[3]) * !(op[2]) * op[1] * op[0]$
	State 10	$op[3] * !(op[2]) * !(op[1]) * !(op[0])$
	State 11	$op[3] * !(op[2]) * !(op[1]) * op[0]$
State 2	State 1	$!(op[3]) * !(op[2]) * !(op[0])) * !(c_i * z_i + c_i * c_f + z_i * z_f))$
	State 3	$((!(op[3]) * !(op[2]) * !(op[0])) * !(c_i * z_i + c_i * c_f + z_i * z_f)) + (op[3] * op[2])$
	State 13	$!(op[3]) * op[2] * op[1] * !(op[0])$
	State 15	$!(op[3]) * op[2] * op[1] * op[0]$
State 3	State 1	$op[3] * op[2] * !(z_f)$
	State 4	$!(op[3]) * !(op[2]) * !(op[1] * op[0])$
	State 10	$op[3] * op[2] * z_f$
State 4	State 1	Unconditional
State 5	State 3	Unconditional
State 6	State 7	$!(op[3]) * op[2] * !(op[1]) * !(op[0])$
	State 8	$!(op[3]) * op[2] * !(op[1]) * op[0]$
State 7	State 4	Unconditional
State 8	State 1	Unconditional
State 9	State 4	Unconditional
State 10	State 1	$op[3] * op[2]$
	State 11	$op[3] * !(op[2]) * !(op[1]) * !(op[0])$
State 11	State 1	$op[3] * !(op[2]) * !(op[1]) * !(op[0])$
	State 12	$op[3] * !(op[2]) * !(op[1]) * op[0]$
State 12	State 1	Unconditional
State 13	State 14	Unconditional
State 14	State 1	$T1_7:0 == 00000000$
	State 13	$(T1_7:0 != 00000000) * !(op[3]) * op[2] * op[1] * !(op[0])$
	State 15	$(T1_7:0 != 00000000) * !(op[3]) * op[2] * op[1] * op[0]$
State 15	State 14	Unconditional

Table 1: Transition logic table

4 Finite State Machine

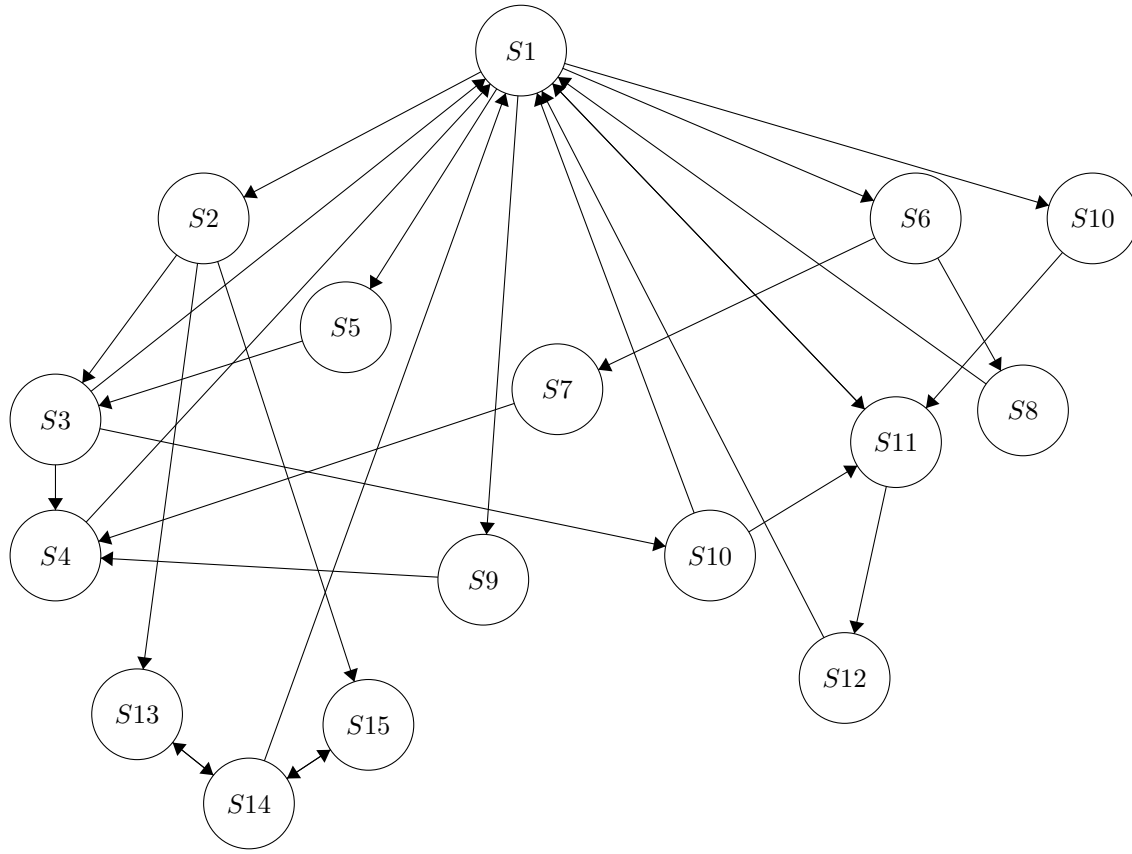

5 Datapath

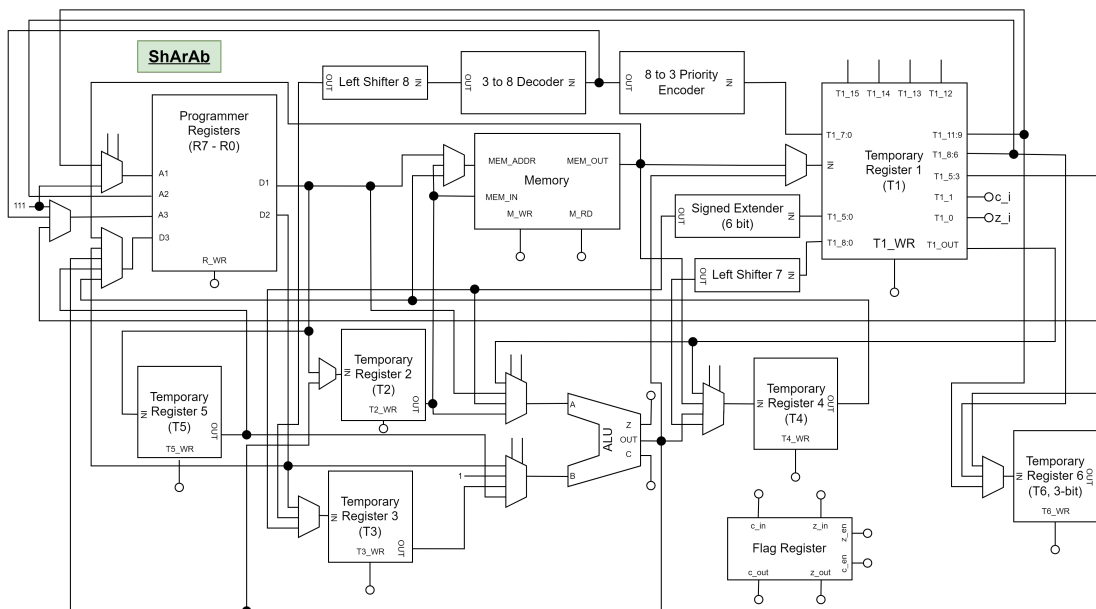


Figure 8: Data Path

5.1 Components used in Data Path

The components used in Data Path are all contained in a package **Components**. The code for the same is given in a [drive file](https://drive.google.com/file/d/1mGKq8yeuYL9Km-GQuibvaU7kGaJ25YWm/view?usp=sharing). (https://drive.google.com/file/d/1mGKq8yeuYL9Km-GQuibvaU7kGaJ25YWm/view?usp=sharing)

5.2 Code implementation of Data Path

For VHDL implementation of the Data Path, the code can be found on [Github](https://github.com/shobman17/IITB-CPU). (https://github.com/shobman17/IITB-CPU)

6 Testing

6.1 CPU definition

Entity CPU combines both the entities FSM and DataPath such that the only input it takes is clk.

```
1  library ieee;
2  use ieee.std_logic_1164.all;
3
4  library Work;
5  use work.Components.all;
6
7  entity CPU is
8      port(clk: in std_logic);
9  end entity;
10
11 architecture complete of CPU is
12     component FSM is
13         port( opcode:in std_logic_vector(3 downto 0);
14               t1_70:in std_logic_vector(7 downto 0);
15               c_i, z_i, z_in, c_out, z_out:in std_logic;
16               clk:in std_logic;
17               output_state: out std_logic_vector(3 downto 0)
18         );
19     end component;
20
21     component DataPath is
22         port(clk: in std_logic; state: in std_logic_vector(3 downto 0);
23               out_c_i, out_z_i,out_z_in, out_c_out, out_z_out: out std_logic;
24               opcode: out std_logic_vector(3 downto 0);
25               t17downto0: out std_logic_vector(7 downto 0));
26     end component;
27
28     for all: Datapath
29         use entity work.Datapath(trivial);
30
31     for all: FSM
32         use entity work.FSM(shatranj);
33
34     signal t17downto0: std_logic_vector(7 downto 0);
35     signal state, opcode: std_logic_vector(3 downto 0);
36     signal c_i, z_i, z_in, c_out, z_out: std_logic;
37
38     begin
39         Main_Data: Datapath
40             port map(clk, state, c_i, z_i, z_in, c_out, z_out, opcode, t17downto0);
41
42         Main_FSM: FSM
43             port map(opcode, t17downto0, c_i, z_i, z_in, c_out, z_out, clk, state);
44     end architecture;
```

CPU_tb is the testbench used for CPU. It gives a clk input with a clock period of 20ns. For testing using this testbench, we hardcoded specific instructions into the Memory storage and Register Files.

6.2 Testing Code

The memory and programmer registers were hard-coded with instructions to test them. The instructions are saved in the submitted code files. Following are the simulation results:

1. ADD R1 R4 R2

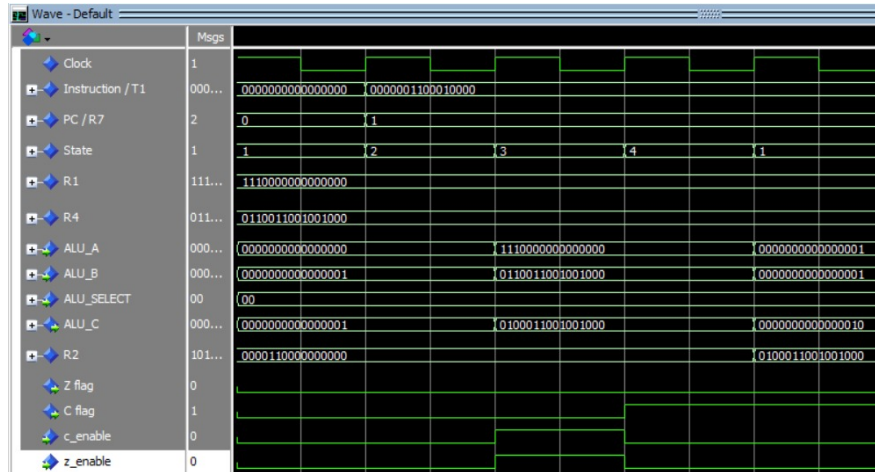


Figure 9: ADD R1 R4 R2

2. ADD R1 R0 R2

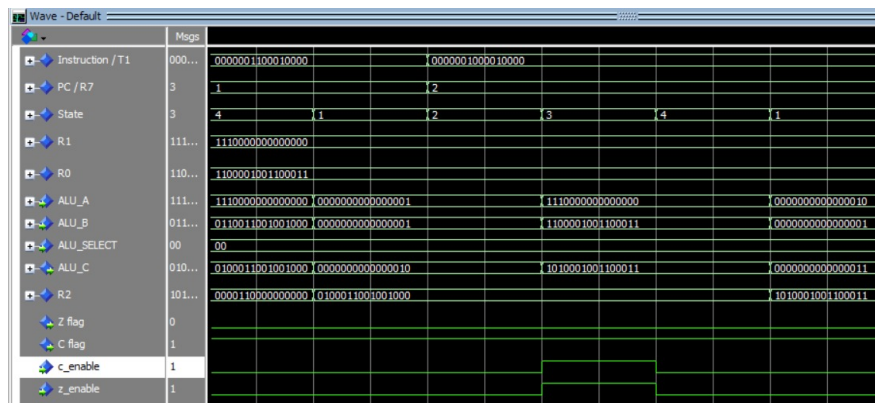


Figure 10: ADD R1 R0 R2

3. ADC R1 R4 R2

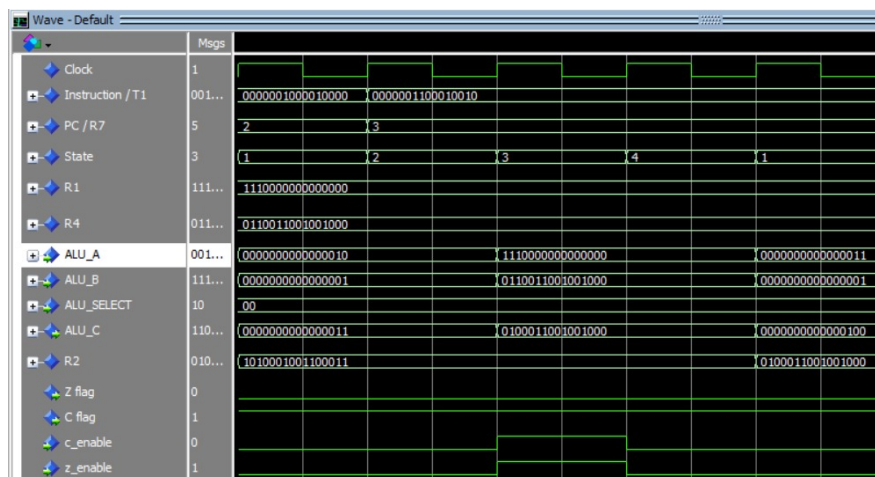


Figure 11: ADC R1 R4 R2

4. ADZ R3 R1 R2

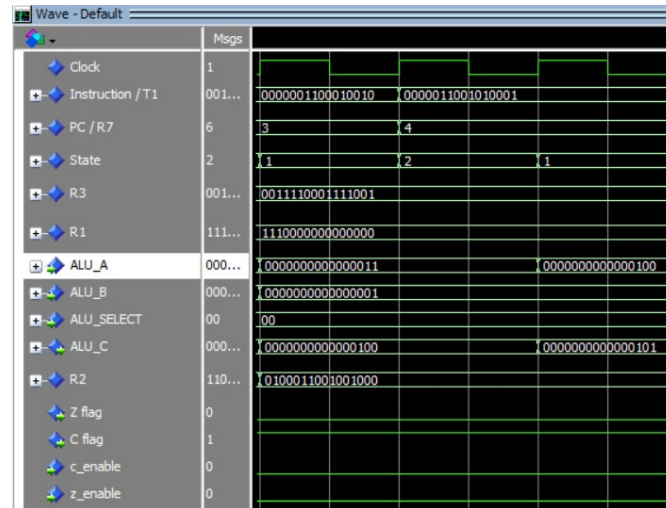


Figure 12: ADZ R3 R1 R2

5. NDU R3 R1 R2

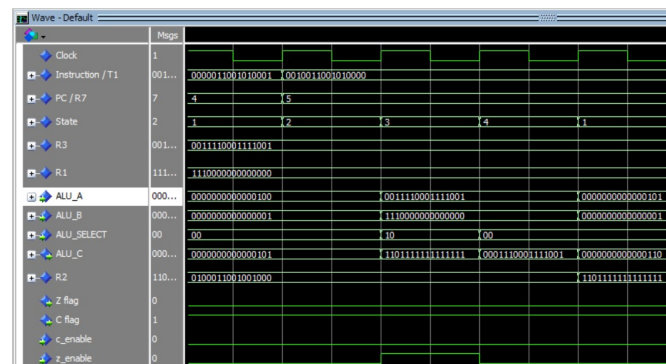


Figure 13: NDU R3 R1 R2

6. NDZ R7 R6 R2

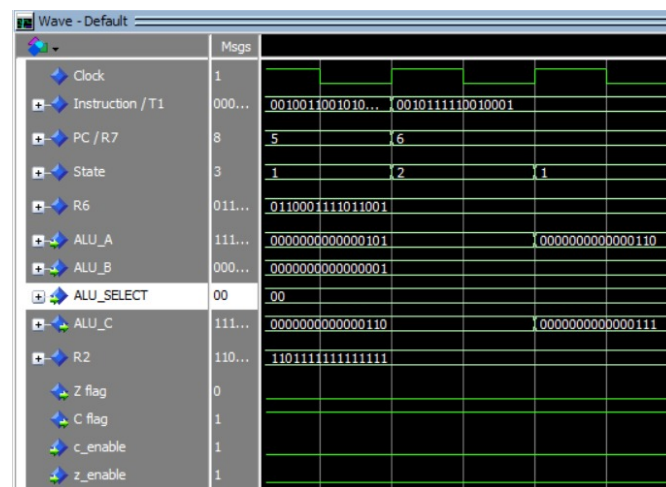


Figure 14: NDZ R7 R6 R2

7. NDC R5 R1 R2

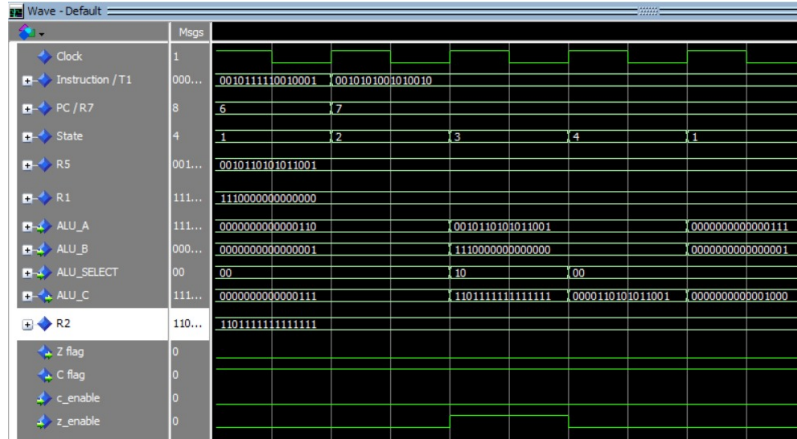


Figure 15: NDC R5 R1 R2

8. ADI R1 R2 010000

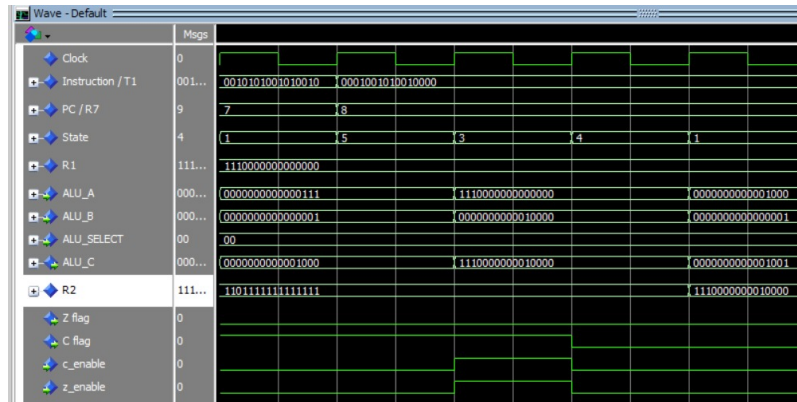


Figure 16: ADI R1 R2 010000

9. LHI R2 100000000

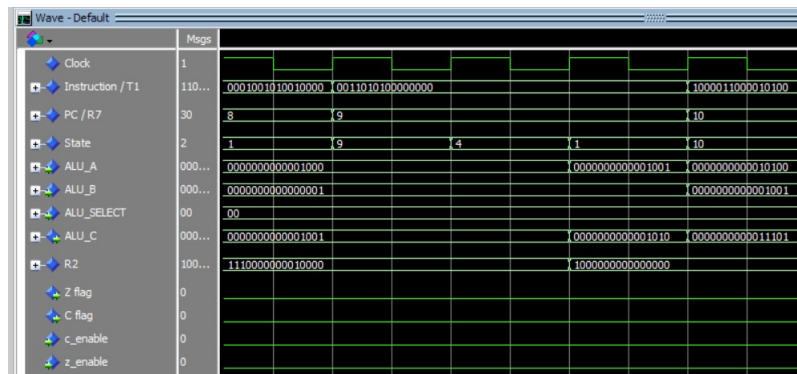


Figure 17: LHI R2 100000000

10. JAL R3 000010100

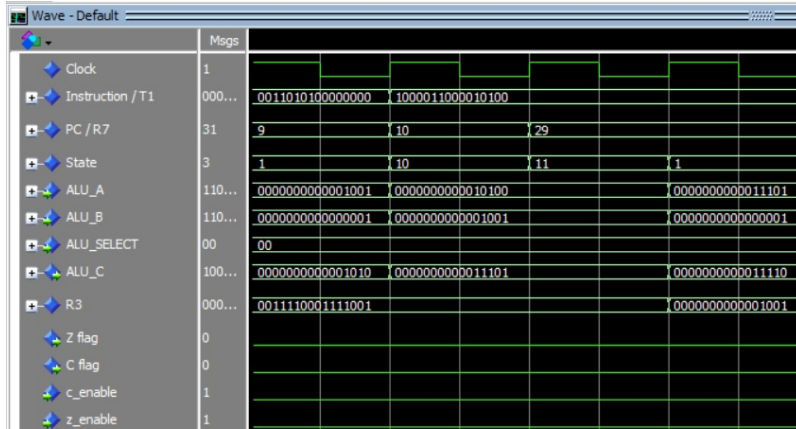


Figure 18: JAL R3 000010100

11. BEQ R3 R3 00000101101

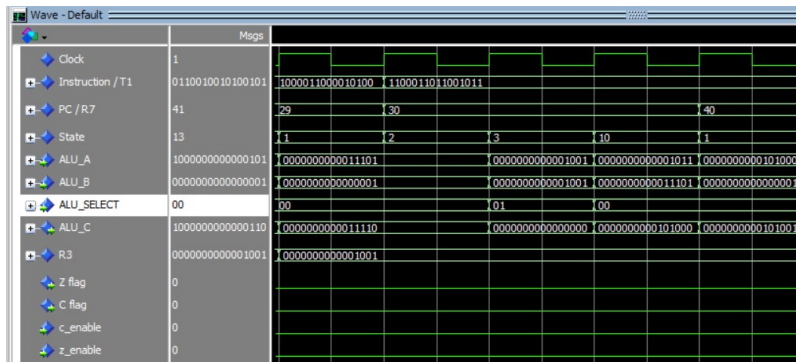


Figure 19: BEQ R3 R3 00000101101

12. LM R2 010101100

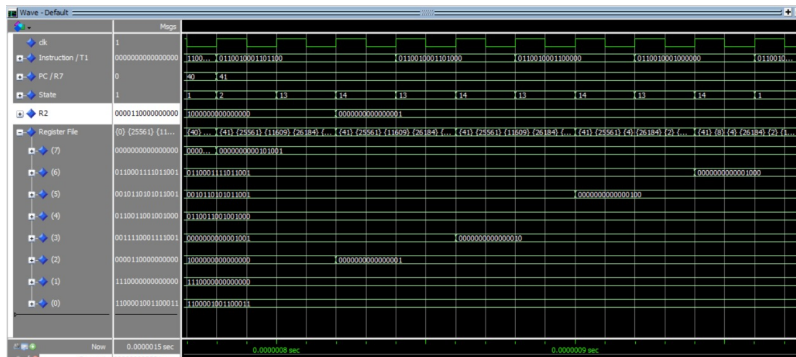


Figure 20: LM R2 010101100

13. SM R3 010101100

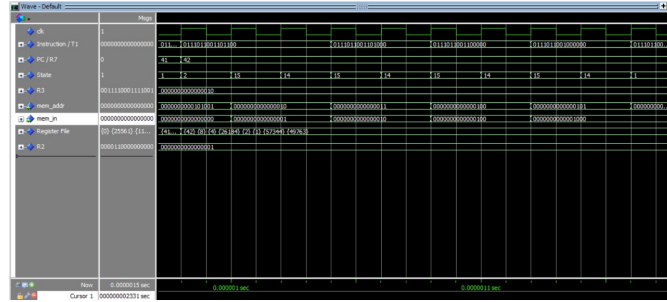


Figure 21: SM R3 010101100

14. SW R1 R2 000001

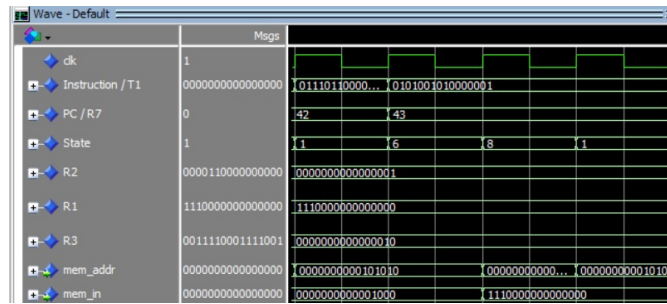


Figure 22: SW R1 R2 000001

15. LW R1 R2 000001

 


Figure 23: LW R1 R2 000001

16. JLR R2 R2 000000

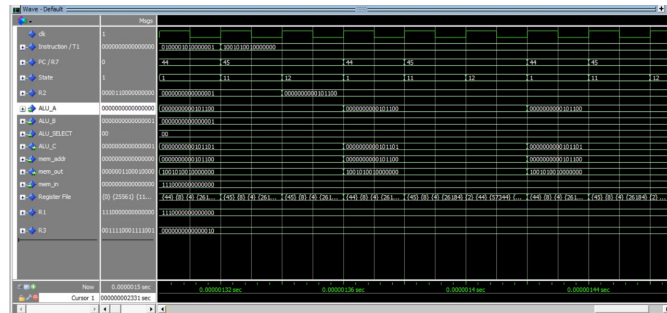


Figure 24: JLR R2 R2 000000

